



We use cookies 🍪

Our websites use cookies (also from third parties) for functional and analytical purposes, and to show you personalised advertisement. You can adjust this in [Cookie Settings](#) or learn more by reading our [cookie policy](#).

ermistor?!



ONLY REQUIRED

ACCEPT ALL

× 1



Resistor 10k ohm

× 1 

Arduino UNO

× 1 

Jumper wires (generic)

× 1 

Breadboard (generic)

× 1 

APPS AND ONLINE SERVICES



Arduino IDE



Arduino Web Editor



ABOUT THIS PROJECT



How easy is it to use a thermistor?!

In this article I will explain how to use a thermistor. First of all, what is it a Thermistor? A **thermistor** is a type of resistor *whose resistance is dependent on temperature*. There are two opposite types of thermistor:

- PTC (**P**ositve **T**emperature **C**oefficient), resistance increases as temperature rises
- NTC (**N**egative **T**emperature **C**oefficient), resistance decreases as temperature rises

In this case I use NTC.

A little bit of math.

To calculate the thermistor resistance using a simple formula called *equation with parameter B* (**with only NTC termistor**).


$$RT = R_0 e^{B \left(\frac{1}{T} - \frac{1}{T_0} \right)}$$

Where:

- e is the base of natural logarithm
- R_0 is the resistance of the thermistor measured at the temperature T_0
- B is a constant coefficient that depends on the characteristics of the

material, it is a constant expressed in K, and its value is indicated by the manufacturers on the technical sheets

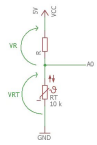To calculate the temperature we need know the resistance R_T using the Ohm's laws.



This is a schematic version of circuit.

$$R_T = V_{RT} / (V_R / R)$$

Now we have all the data to calculate the temperature.

$$T = \frac{1}{\frac{\ln(\frac{R_T}{R_0})}{B} + \frac{1}{T_0}}$$

Remember to convert all parameters (for example T_0) to Kelvin before the calculations, and also the result is in Kelvin.

This is the result.



CODE

Thermistor Arduino





```
1 //Thermometer with thermistor
2
3 /*thermistor parameters:
4  * RT0: 10 000  $\Omega$ 
5  * B: 3977 K +- 0.75%
6  * T0: 25 C
7  * +- 5%
8  */
9
10 //These values are in the datasheet
11 #define RT0 10000 //  $\Omega$ 
12 #define B 3977 // K
13 //-----
14
15
16 #define VCC 5 //Supply voltage
```

SCHEMATICS

termistore_bb.jpg

DOWNLOAD

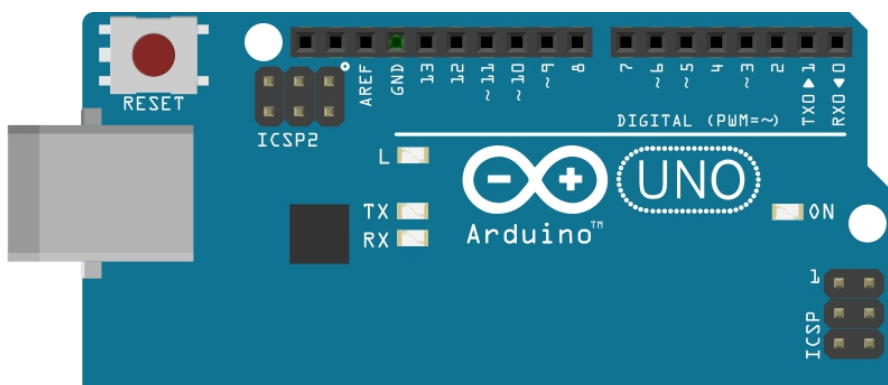


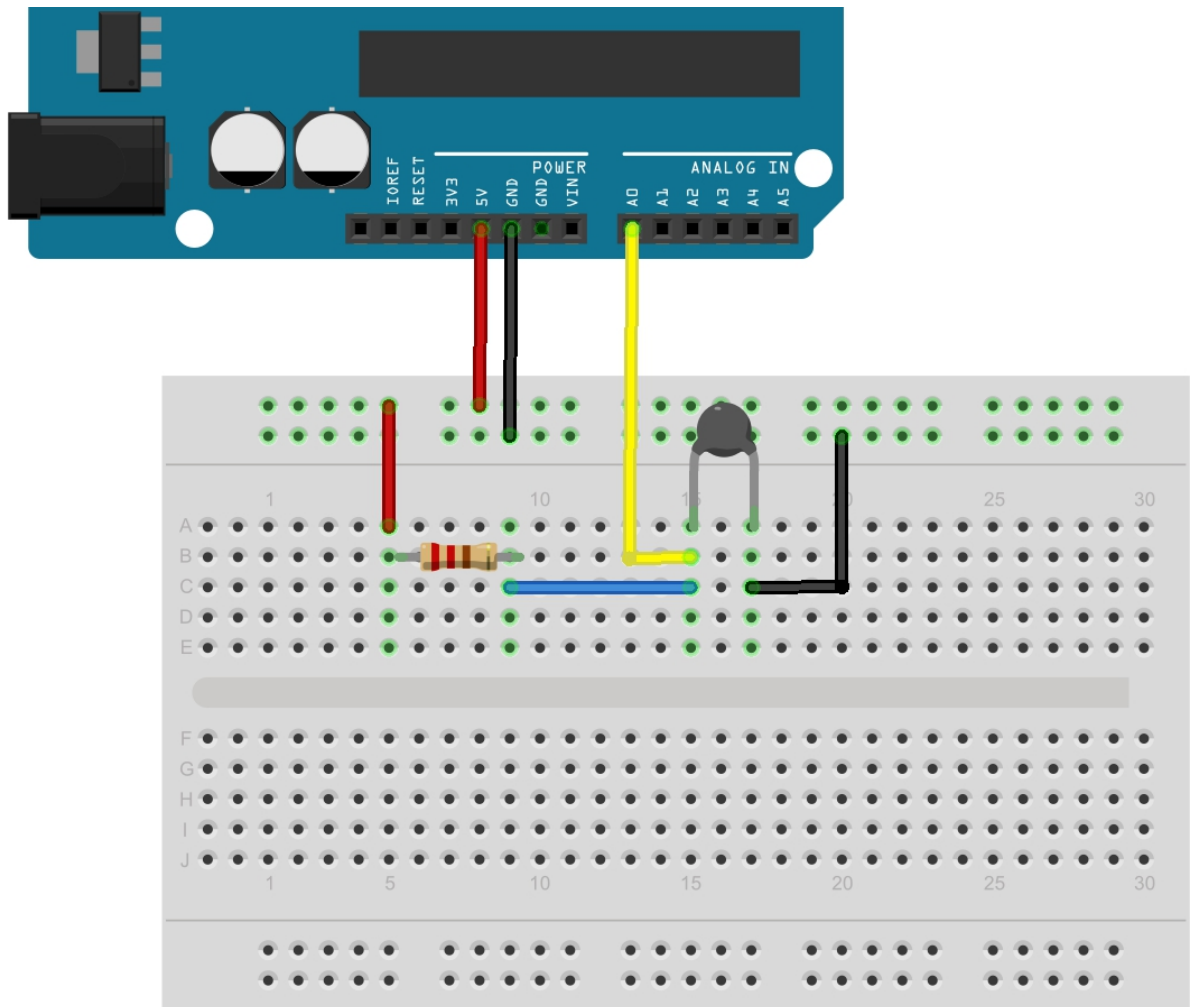


fritzing

termistore_schem.jpg

DOWNLOAD

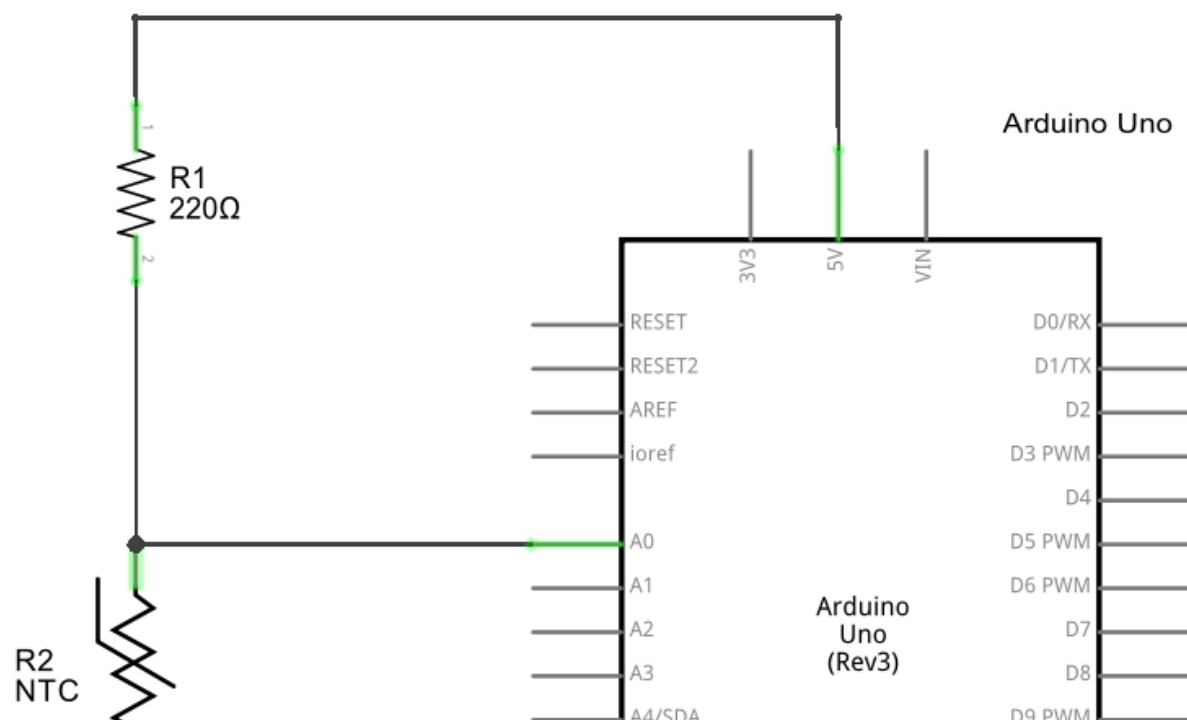

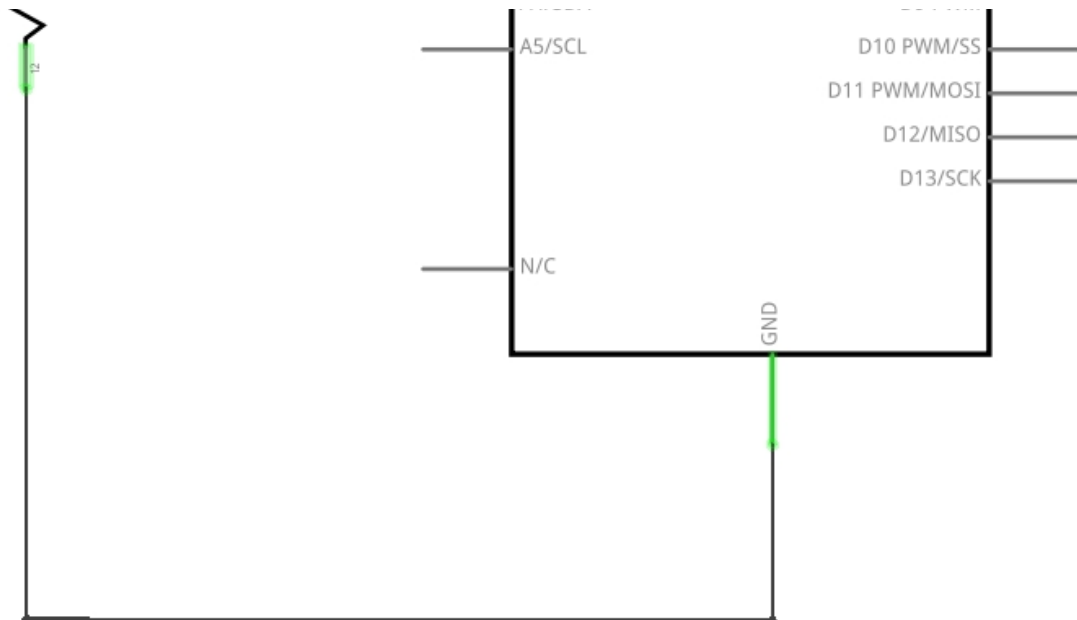

fritzing

COMMENTS



Please [log in](#) or [sign up](#) to comment.



Arnov Sharma

2 years ago

Ma ma mia very naice



Praneshvar_4767

2 years ago

How to calculate resistance of thermistor



aigless

2 years ago

Your code not work. I tried the temperatures goes inverted.
i tried panstamp library and works. what's wrong?
panStamp library contact@panstamp.com



Viiliainen

2 years ago

This works only for NTC.
For PTC you need to create polynome or function like this :
<https://www.schmidt-welt.net/weblog/arduino-and-kty81-210/>
..with parameters matching your sensor.



Binary_Designer

2 years ago

Thank you very much! It was very nicely explained and worked right away.



waldenjryan

a year ago

Hi there the schematic shows a 220 resistor. Unless i'm mistaken (an i often am) i think it should be a 10K resistor

1 thank

AUTHOR



Marcazzan_M

7 PROJECTS 54 FOLLOWERS

FOLLOW

PUBLISHED ON

November 14, 2016

 RESPECT PROJECT

 WRITE A COMMENT

 Share

MEMBERS WHO RESPECT THIS PROJECT



and 12 others

SIMILAR PROJECTS YOU MIGHT LIKE

Unr...

Project in progress by **ExeCuteLi**

27,645 VIEWS **27** COMMENTS **50** RESPECTS

Easy...

Project tutorial by **hixel**

3,279 VIEWS **1** COMMENT **5** RESPECTS

Easy...

Project showcase by **Marcazzan_M**

23,215 VIEWS **4** COMMENTS **26** RESPECTS

Ardu...

Project tutorial by **David Escobar**

18,364 VIEWS **4** COMMENTS **46** RESPECTS

Hac...

Project tutorial by **Katie Kristoff**

1,488 VIEWS **3** COMMENTS **9** RESPECTS

Easy...

Project tutorial by **ElectroPeak**

93,070 VIEWS **14** COMMENTS **375** RESPECTS



Powered by
hackster.io